

問題 2

MOS ランジスタは非線形特性があるため、動作の解析が困難である。そこで、バイアス点の近傍の微小範囲で解析を行う。この手法を小信号解析と呼ぶ。短チャネル MOS ランジスタの小信号モデルは図 1 のように書ける。ただし、基板バイアス効果を無視する。また、相互コンダクタンスを g_m 、トランジスタの出力抵抗を r_o 、ゲート・ソース間電圧の小信号成分を v_{gs} とする。記号は凡例に従う。以下の間に答えよ。

- (1) 図 2 のように抵抗負荷 R_D を付けたソース接地回路の小信号等価回路を示せ。さらに、電圧増幅率 A_V 、入力抵抗 R_{in} 、出力抵抗 R_{out} を式で示せ。
- (2) 図 3 は、図 2 の抵抗負荷 R_D の代わりに定電流源を付けたソース接地回路である。この回路の小信号等価回路を示せ。また、電圧増幅率 A_V を式で示せ。
- (3) 定電流源の作り方として、図 4 のような回路を使うことが考えられる。この時の小信号等価回路を示せ。また、電圧増幅率 A_V を式で示せ。
- (4) 図 5 のような回路を使って、図 4 における定電流源としての MOS にゲートバイアス V_b を与える。この回路では、 I_{in} と同じ大きさの電流をいつでも I_{out} に流すことができる。このことに着目し、図 6 の差動增幅回路の差動ゲインを求めよ。
- (5) 図 7 のように差動增幅回路に容量で帰還を掛ける。この差動增幅回路の閉ループゲインを求めよ。

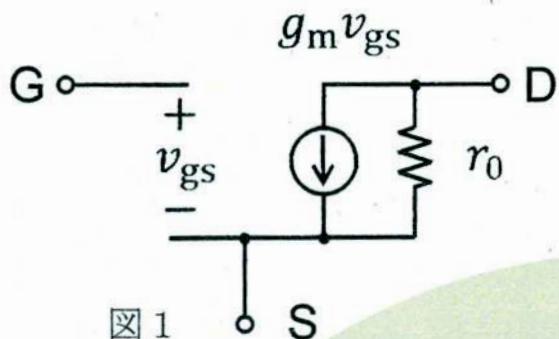


図 1

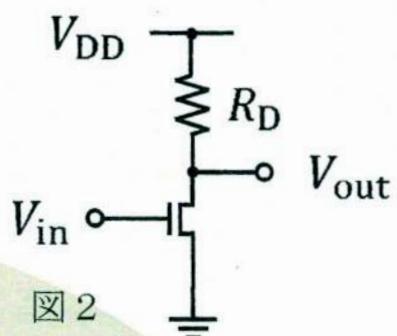


図 2

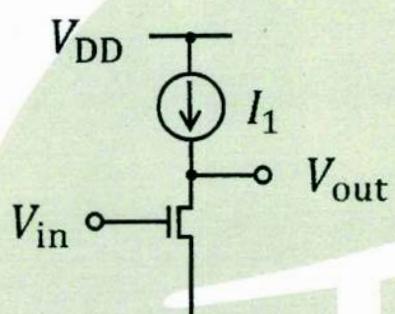


図 3

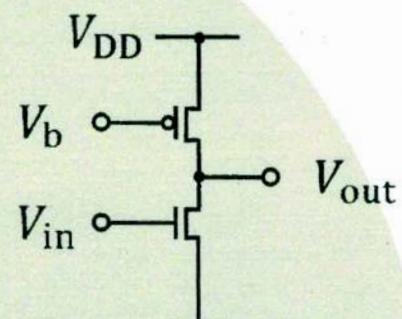


図 4

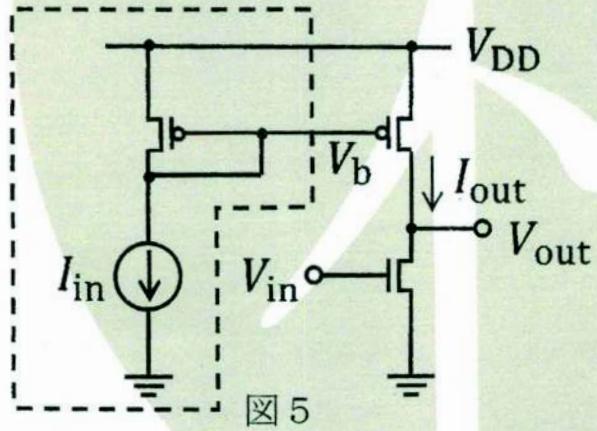


図 5

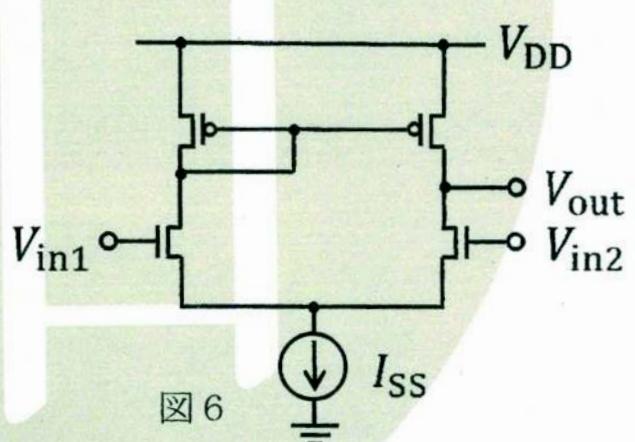


図 6


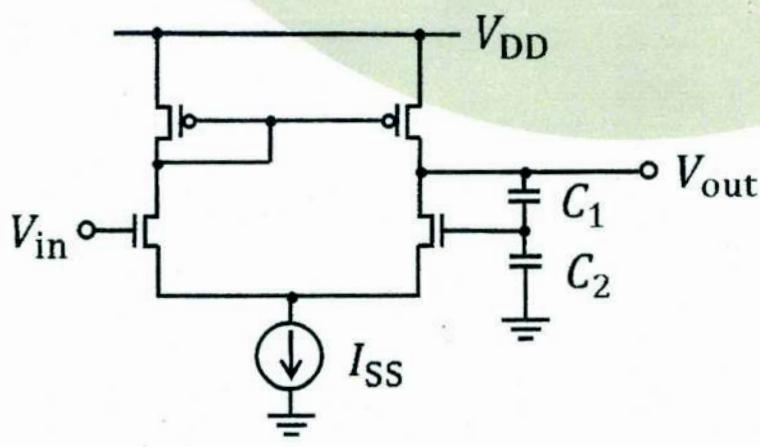


図 7

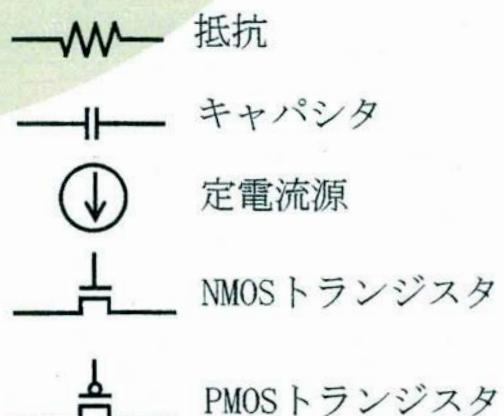

凡例

Problem 2

Because of the non-linear characteristics of MOS transistors, it is difficult to analyze their operation. Therefore, a minute range in the vicinity of the bias point is analyzed. This is referred to as the small-signal analysis method. Figure 1 shows the small-signal model of a short-channel MOS transistor. Here, the substrate bias effect is neglected, and let g_m be the transconductance, r_0 be the output resistance, and v_{gs} be the small signal component of the gate-to-source voltage. Symbols in the figures can be found in the legend. Answer the following questions.

- (1) Draw the small-signal equivalent circuit of the common-source circuit with a load resistance R_D as shown in Fig. 2. In addition, express the voltage gain A_V , the input resistance R_{in} , and the output resistance R_{out} .
- (2) Figure 3 shows the common-source circuit after replacing R_D in Fig. 2 with a constant current source. Draw the small-signal equivalent circuit for it. In addition, find a formula for the voltage gain A_V .
- (3) A constant current source can be realized by a circuit shown in Fig. 4. Draw its small-signal equivalent circuit. In addition, find a formula for the voltage gain A_V .
- (4) The circuit shown in Fig. 5 is used to provide a gate bias V_b of the MOS transistor as a constant current source in Fig. 4. In this circuit, the current I_{out} is always equal to I_{in} . Taking this into account, show the differential gain of the differential amplifier circuit shown in Fig. 6.
- (5) As shown in Fig. 7, feedback is applied to the differential amplifier circuit by using the capacitors. Find the closed-loop gain of this differential amplifier circuit.

