

問題 2

以下の問に答えよ。図中の記号は凡例に従う。 ω は角周波数、 t は時刻を表す。必要であれば図1の角度を用いよ。

(1) 図2に示す回路について以下の問(1-1)から問(1-5)に答えよ。

(1-1) 電流 $i(t)$ を求めよ。

(1-2) 電圧 $v_R(t)$, $v_L(t)$, $v_C(t)$ を求めよ。

(1-3) 図3のフェーザ図に交流電圧源 $v_s(t)$ のフェーザ V_s が示されている。図3を解答用紙に書き写し、 $v_R(t)$, $v_L(t)$, $v_C(t)$ のフェーザを描け。

(1-4) 有効電力 P , 無効電力 Q , 皮相電力 S , 力率 PF を求めよ。

(1-5) 図2に示す回路の a-b 間に素子を1つ挿入すると力率が1になった。その素子の種類と値を答えよ。

(2) 図4に示す回路において抵抗 R_L が最大電力を消費するとき、 R_L の値と最大電力を有効数字2桁で求めよ。なお、図4の中の理想変圧器は巻き数比が4:1である。

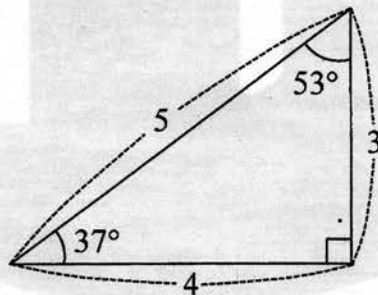
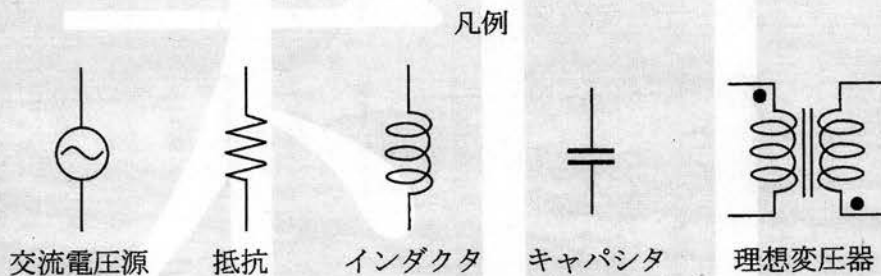


図1

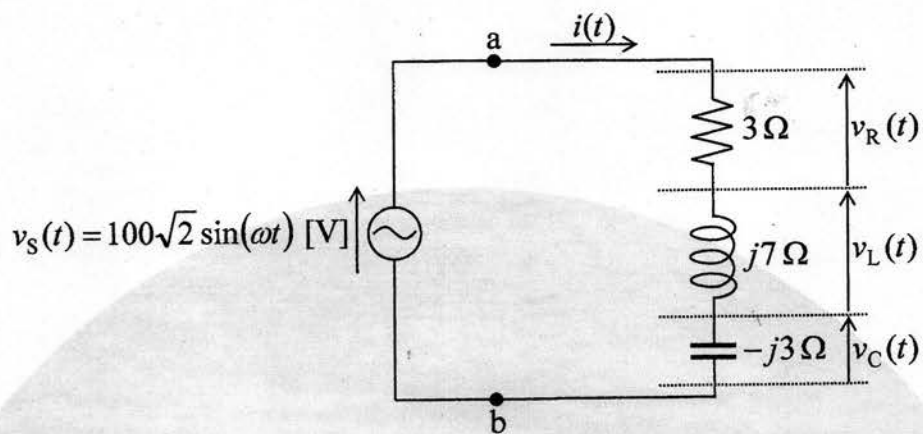


图 2

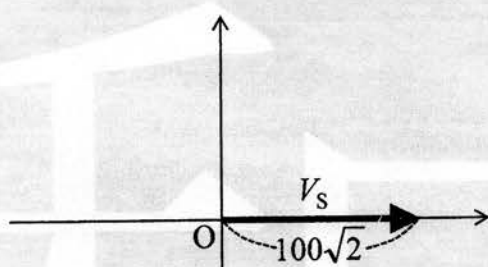


图 3

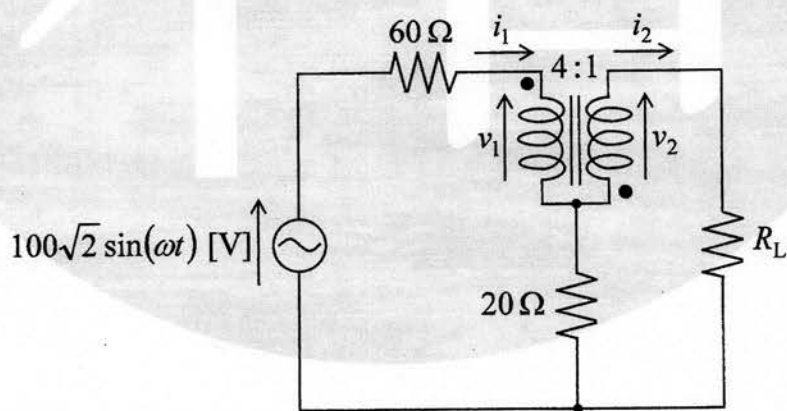


图 4

Problem 2

Answer the following questions. Symbols in the figures can be found in the legend. ω is the angular frequency and t is the time. If necessary, use the angles in Fig. 1.

(1) Answer the following questions from (1-1) to (1-5) on the circuit shown in Fig. 2.

(1-1) Find the current $i(t)$.

(1-2) Find the voltages $v_R(t)$, $v_L(t)$, and $v_C(t)$.

(1-3) Phasor V_S of the AC voltage source $v_S(t)$ is shown in the phasor diagram in Fig. 3.

Copy Fig. 3 to the answer sheet and draw the phasors of $v_R(t)$, $v_L(t)$, and $v_C(t)$.

(1-4) Find the active power P , the reactive power Q , the apparent power S , and the power factor PF .

(1-5) When an element is inserted between a and b in the circuit shown in Fig. 2, the power factor of 1 is achieved. Determine the type of the element and its value.

(2) When the resistor R_L consumes the maximum power in the circuit shown in Fig. 4, determine the value of R_L and the maximum power with two significant digits. The ideal transformer in Fig. 4 has the turns ratio of 4:1.

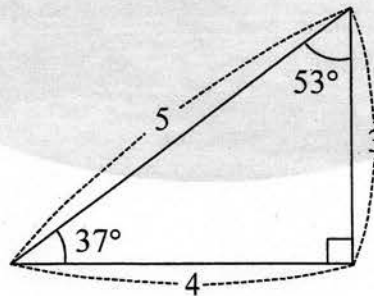
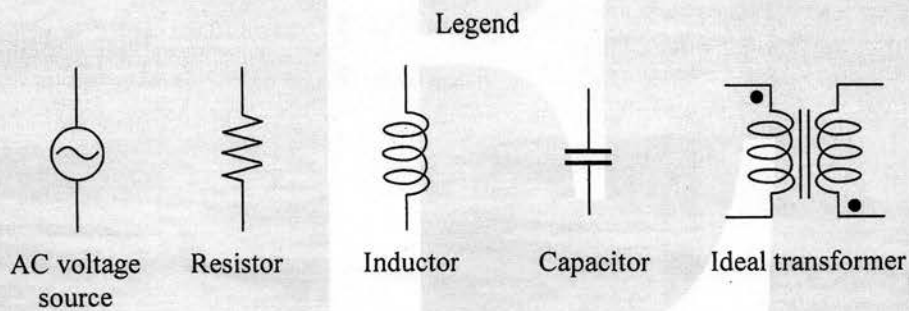


Fig. 1

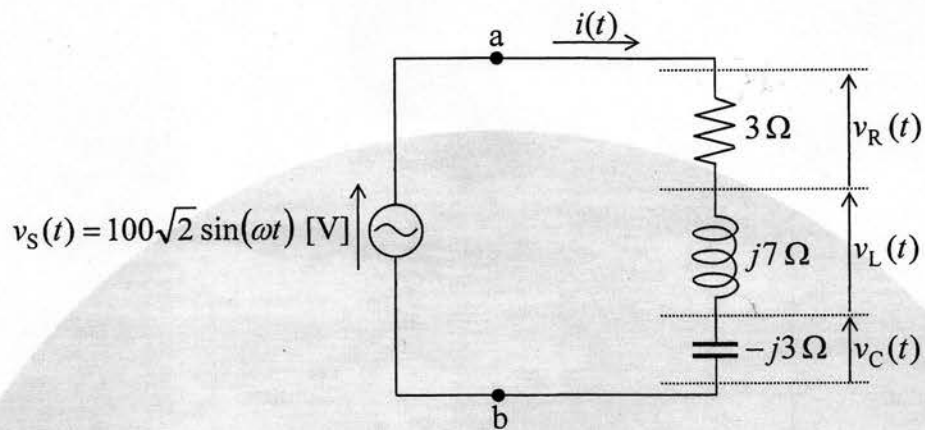


Fig. 2

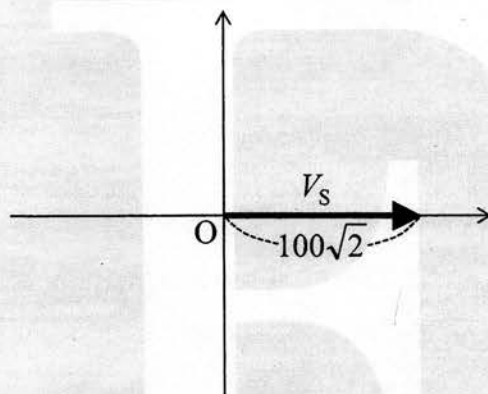


Fig. 3

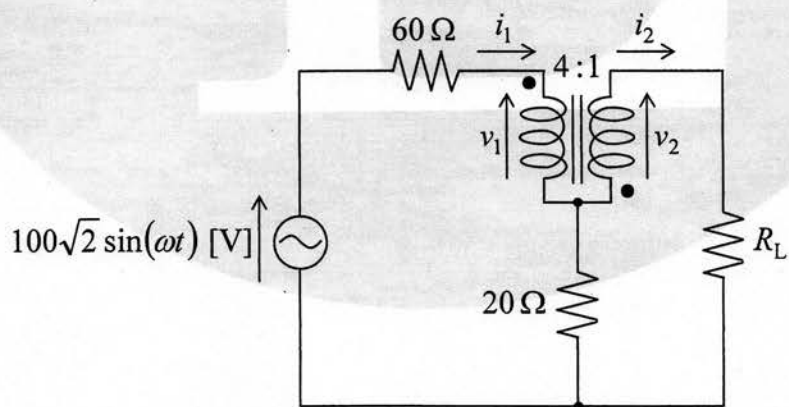


Fig. 4